

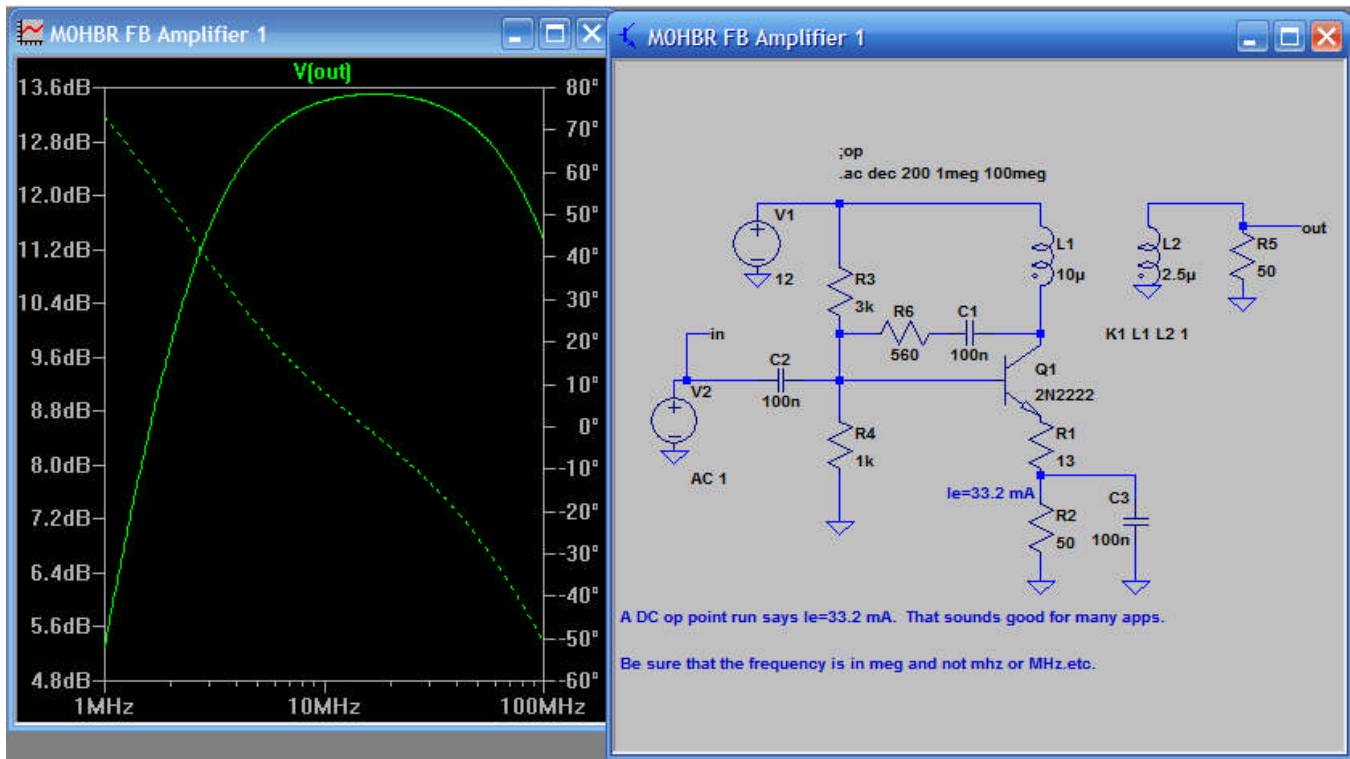
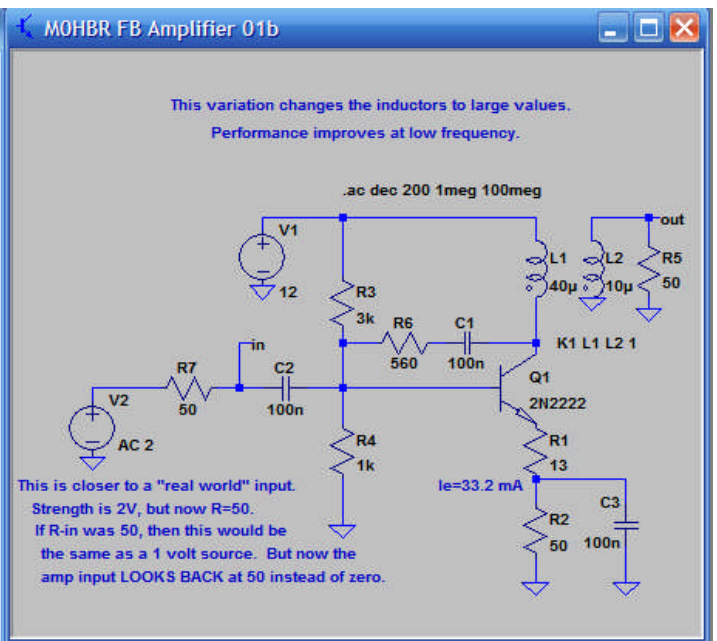
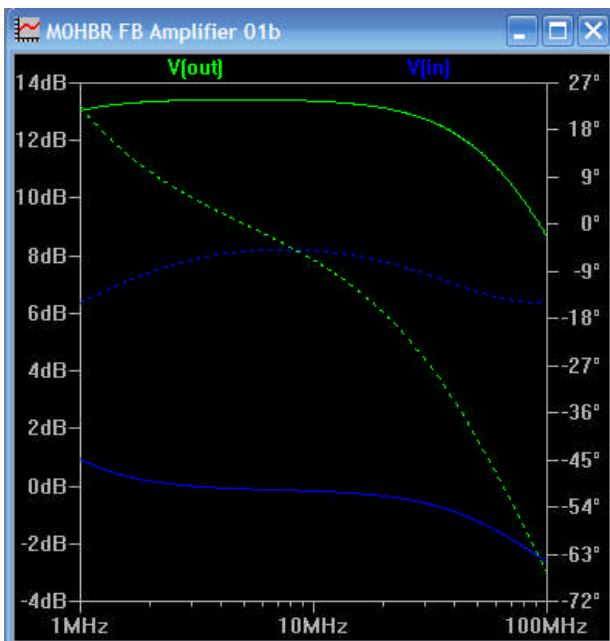



Basic Amplifier Analysis in SPICE Wes Hayward, w7zoi, 12Jan07

This is a collection of simulations done to investigate a very basic feedback amplifier. The circuit includes both emitter degeneration and collector-to-base resistance. The development is presented in an evolution aimed at illustrating the methods. Generally, we will just insert the figures. Comments within them will then present most material.


The simulations were all done with SWCad, a wonderful SPICE program offered by Linear Technology, Inc. I highly recommend the program to those wanting to do SPICE simulations. However, I urge the user to consider a personal observation that developed over 13 years of integrated circuit design with SPICE and other programs: **The Simulation is the Greater Experiment.** That is, the results are only as good as the models and the completeness of the simulation files. The *real truth* lies with experimental results.

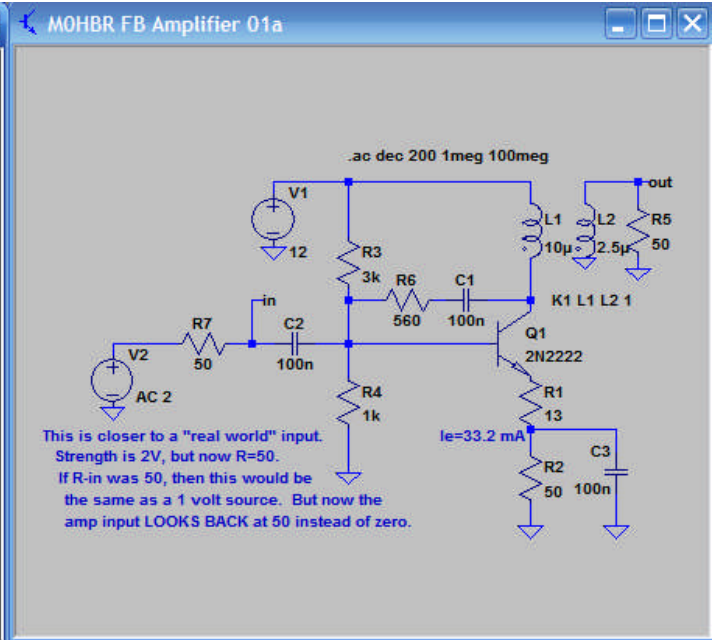

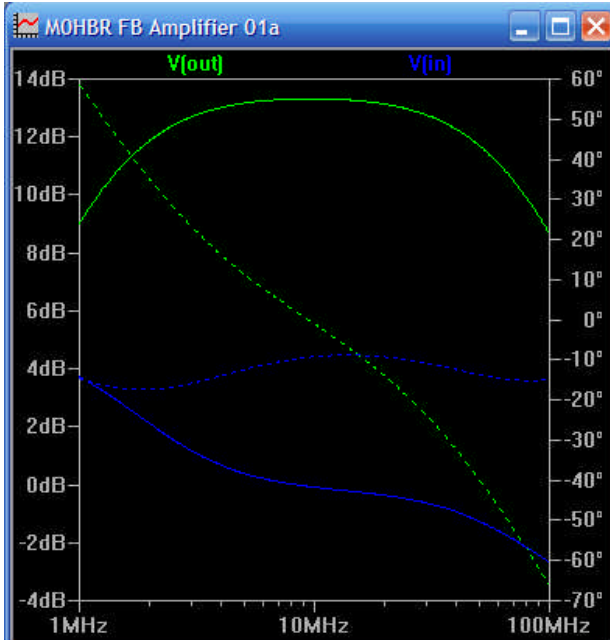

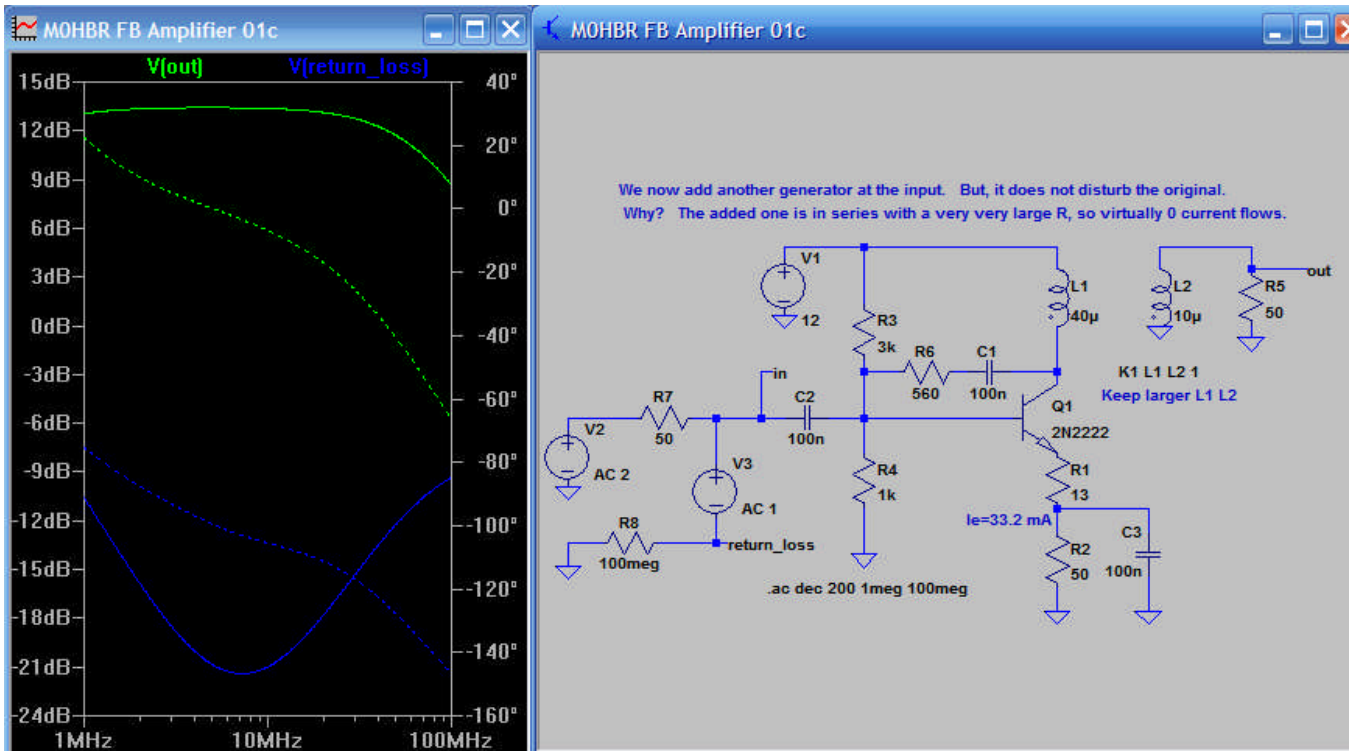

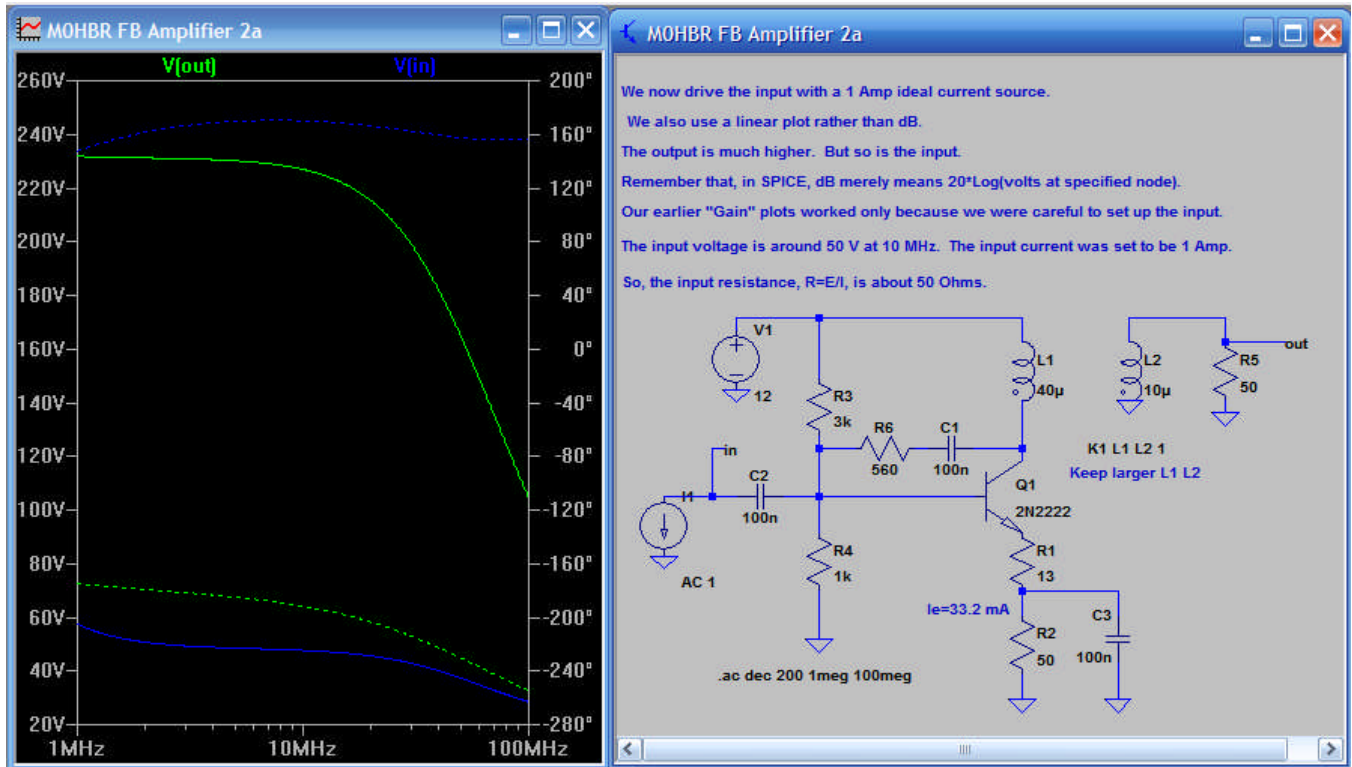The methods used here are described in greater detail in "Reflections on the Reflection Coefficient: An Intuitive Examination," QEX, January, 1993. The point labeled "return loss" should formally be named "S11" or "gamma". In dB form, it is the negative of return loss.



The input impedance is easily calculated from Ohm's Law:


Impedance calculations

The voltage is 47.69 at 170.2 degrees. The current is 1 Amp, but it is *out* of the amplifier, so has phase of 180 degrees. The impedance is then the ratio, 47.69 with a phase of -9.8 degrees.

$$Z = A \cdot (\cos(\theta) + j \cdot \sin(\theta))$$

$$A := 47.69 \quad \theta := \frac{-9.8 \cdot \pi}{180} \quad \theta = -0.171 \quad \text{radians}$$

$$\text{So, } Z = 46.99 - j \cdot 8.12$$

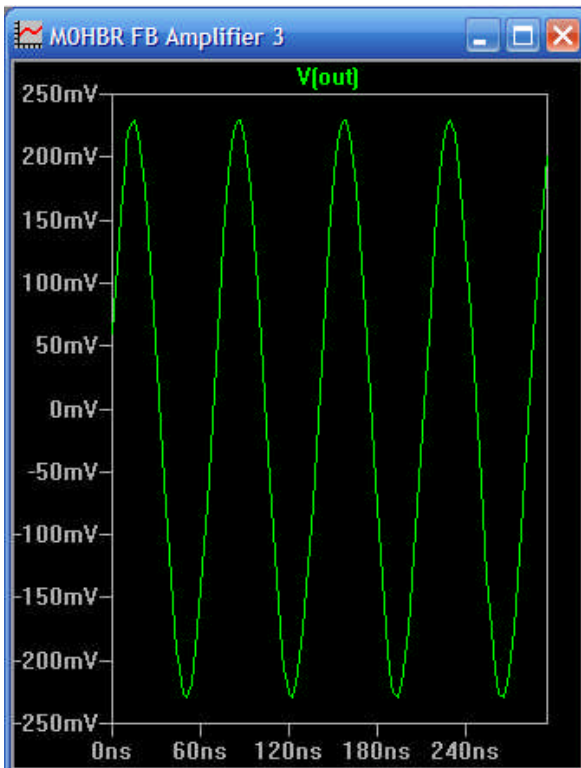

MOHBR FB Amplifier 3


We now want to start to see distortion as well as gain. We use a TRAN analysis. Set the input PEAK drive (SPICE works with peak values) as a parameter with `.param ampl .1` This is the open circuit value. It would be 50 mV across a 50 Ohm load. The peak output is larger at 229 mV. We compare this with an input of 50 mV peak. Voltage gain = $229/50 = 4.58$. $20 \cdot \text{Log}(4.58) = 13.2$ dB. That's familiar.

SINE(0 {ampl} 14meg 0 0 1000)

`.tran 0 10.3u 10u 10n`

`ie=33.2 mA`

K1 L1 L2 1
Retain larger L1 L2

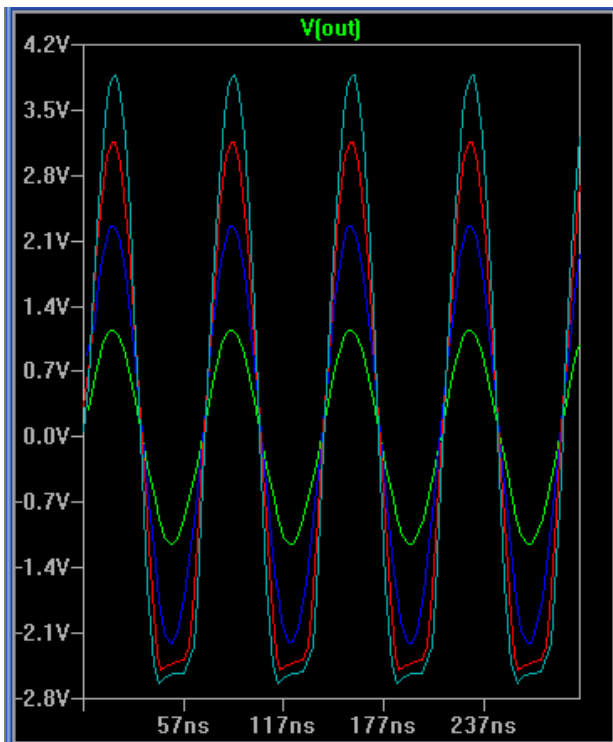

Let's now take advantage of "ampl" as a parameter with a stepped sweep of amplitude. We will go from 0.5 to 2 in 0.5 volt steps. `.step param ampl 0.5 2 0.5`

Distortion appears with higher drives.


SINE(0 {ampl} 14meg 0 0 1000)

`.param ampl .1`



`.tran 0 10.3u 10u 10n`

`ie=33.2 mA`


K1 L1 L2 1
Retain larger L1 L2

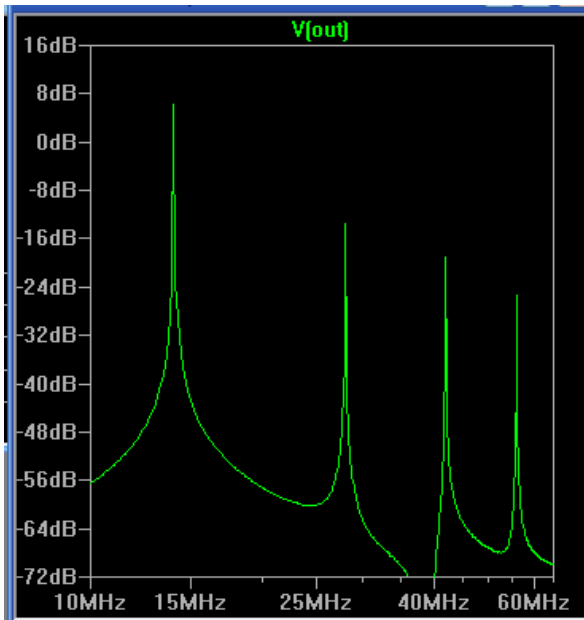


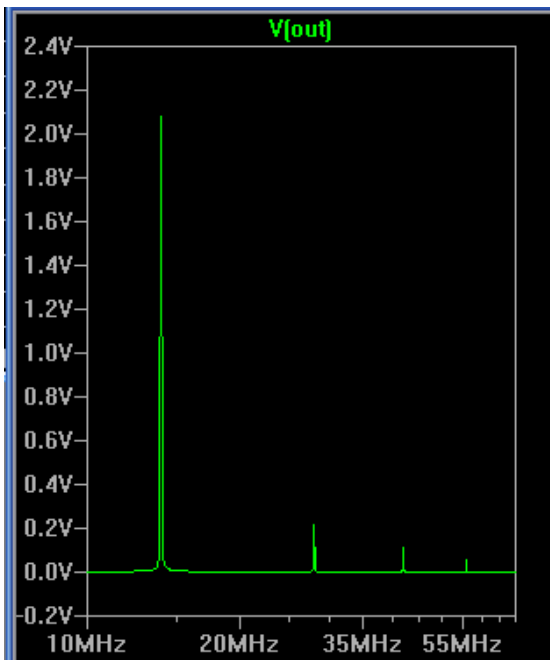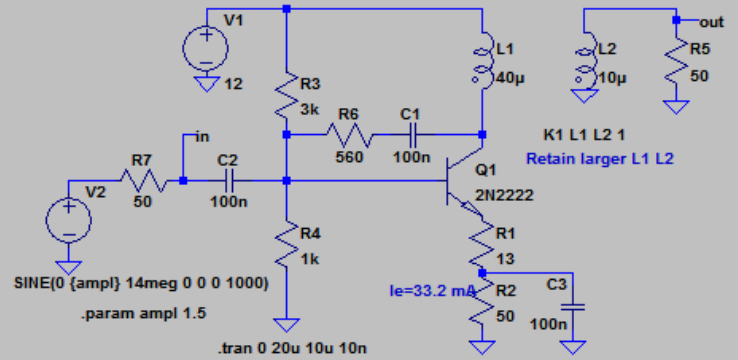We get rid of the sweep, set the drive at 1.5 (where there was distortion) and do a longer sweep. The TRAN run is now to 20 uS, but we only use the last 10 uS of data. Take the full 10 uS of data, and perform a FFT on it to get the dB plot shown. The cursor tells us the peak is 6.3 dB (14 MHz) and the 2nd harmonic is at -13.1 dB. So, the 2nd harmonic is at -19.4 dBc.



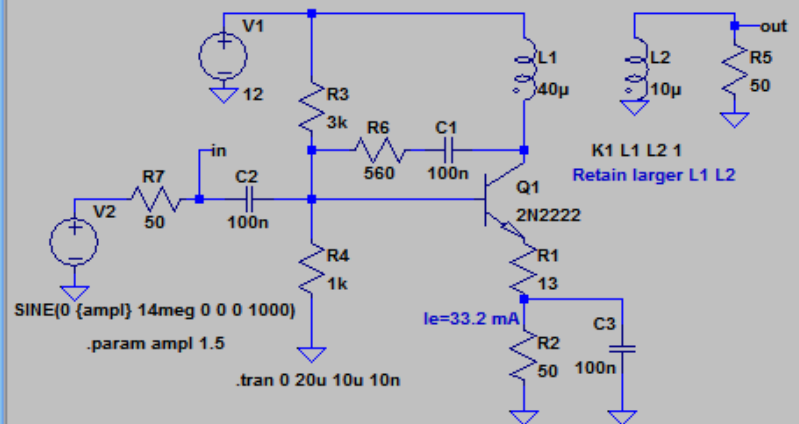We now switch to a linear display (Manual Limits) and measure the voltage at 14 MHz. It is 2.08 V peak. The max drive for this case is 0.75. So gain is 2.773, or 8.9 dB. This is SEVERE. The gain compression is over 4 dB.



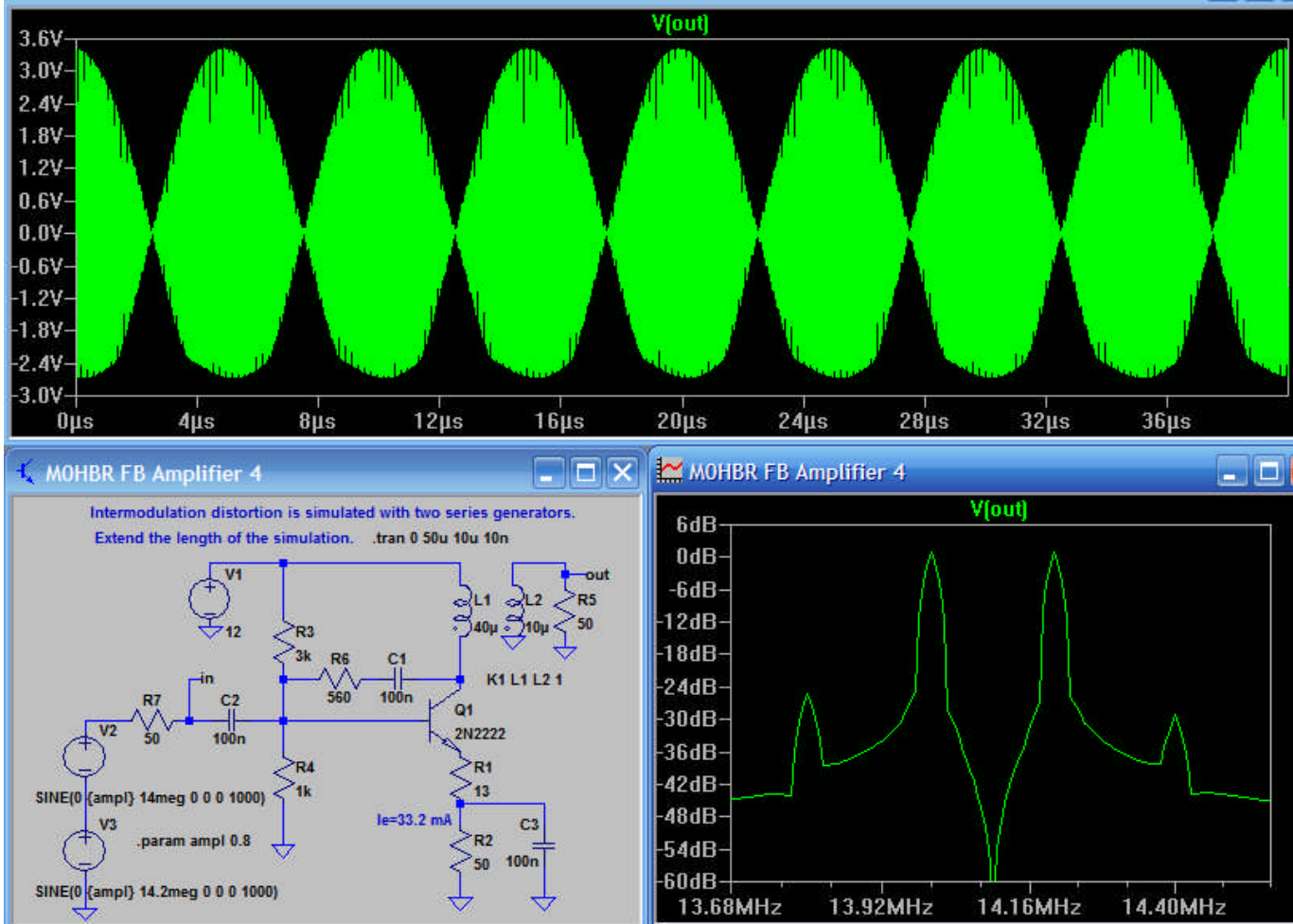

The spectrum plot shown above, lower right, was converted from a dB form to a linear presentation. We then put the cursor on the left major peak to read the voltage as 1.13 Volts. This is a peak value. Power is easily calculated, allowing the output intercept, OIP3, to be evaluated.

$$P = \frac{V_p^2}{2 \cdot R_{Load}} = \frac{1.13^2}{100} = 0.0128 \text{ Watts, or } +11.1 \text{ dBm}$$

$$OIP_3 = P_{out} + \frac{IMDR}{2}$$

$$OIP_3 = 11.1 + \frac{26.5}{2} = 24.3 \text{ dBm}$$

